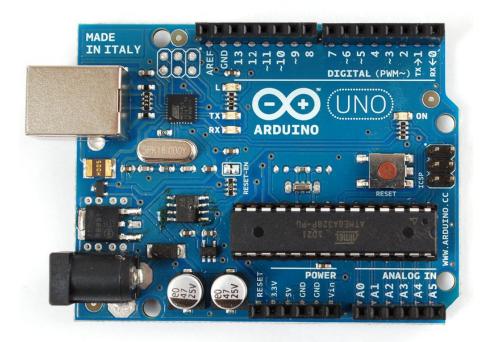


- Search Adafruit
- SHOP
- BLOG
- LEARN
- **FORUMS VIDEOS**
- SIGN IN
- CLOSE MENU

#### 0 Items Sign In



- SHOP BLOG
- LEARN
- FORUMS VIDEOS



# Arduino Tips, Tricks, and Techniques

Get the most out of your Arduino

- Arduino UNO FAQ
- Arduino Libraries
- Bootloader
- Upgrade 3.3V Conversion Arduino Hacks
- ArduinoISP
- Support Forums
- Single Page Download PDF

## Contributors

lady ada Tyler Cooper Feedback? Corrections?
LEARN ARDUINO

## 3.3V Conversion


by Tyler Cooper

# Introduction

All official Arduinos run on 5 volts, which for a long time was the 'standard' voltage for hobbyist electronics and microcontrollers. But now the coolest new sensors, displays and chips are 3.3V and are not 5V compatible. For example, XBee radios, and SD cards and acellerometers all run on 3.3V logic and power. If you tried to connect to them with 5V you could damage the internals of the accessory.

We use chips like the CD4050 to do level conversion but if you are using a lot of 3.3V devices, maybe you're just better off upgrading the entire Arduino to run from 3.3VI

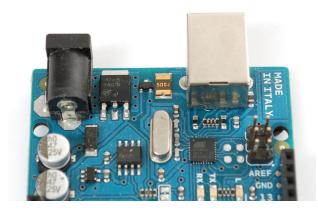To do that, we will replace the regulator so that the DC barrel jack goes to a 3.3v type regulator, not a 5V. And then reconfigure the 5V usb power line so it goes through the regulator as well.




# Replace the Regulator

The default regulator is a 5.0V type, but we want 3.3V out, so we'll need to replace it. We'll use a 1117-3.3V (there are a few manufacturers of 1117 regulators, just like the 7805 is made by many factories) regulator in a TO-252-3 package. It looks like this:



You can get these from any electronics component shop, for example here is the digikey link.

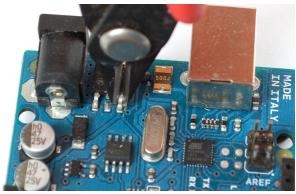To start, we'll need to remove the old regulator. The easiest way to do that is to first clip the two legs.




Then you'll need to heat the tab up to get it liquid so you can lift off the old part. Although it may seem counter intuitive, its best to add some solder to the tab, melt it on with your iron, this will improve the heat conduction since the tab is so large.






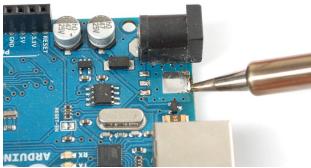
Clean up the tabs and remove any clipped parts still stuck on.



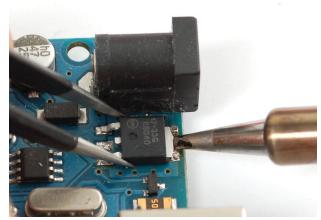Now line up the new 3.3V regulator, and solder the tab first, use plenty of solder and be patient, the tab acts like a heat sink.



Then do the two legs.

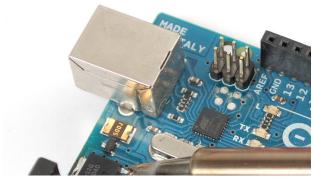

https://learn.adafruit.com/arduino-tips-tricks-and-techniques/3-3v-conversion



# Replacing the Fuse


The next part is a little tricky, the USB jack gives us exactly 5V already, and normally that is tied to the output of the voltage regulator (essentially, its got a little circuitry that connects it when the DC jack is not powered).

The easiest way to make the USB 5V also go through the regulator is to remove the fuse and solder a diode from the USB output to the regulator input.

You can use any power diode, a 1N4001 is perfect and only a few pennies.


The trade off is now there is no 500 mA fuse for the USB jack. The good news is that computers will have their own fuses on the USB connector (inside the computer) so its not likely you will destroy your PC. But be aware that you're losing a little safety.

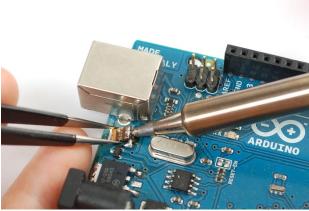Heat the fuse with your soldering iron, again adding solder may help thermal conductivity. Since the fuse is very conductive you can probably just heat one side for a while and both ends will melt.



Clip the diode short and bend the leads over. Solder the side without a stripe (anode) to the old fuse pad, nearest the board edge. Solder the striped end (cathode) to the right hand leg of the regulator.

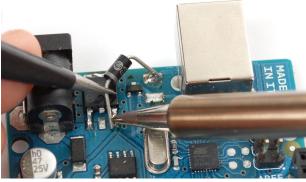The Arduino will still automatically select whichever power plug is giving you more power.



That's it! You are now 3.3V powered. This is a little lower than the power/frequency specification for the AVR chips since they ought to have about 3.6V to run 16Mhz but its *probably* not going to be an issue since AVRs can be overclocked a little.

Last updated on 2015-05-04 at 04.27.26 PM Published on 2013-01-12 at 05.00.13 PM





Arduino Uno R3 (Atmega328 - assembled)



Arduino bootloader-programmed chip (Atmega328P) \$5.95 Add To Cart ADD ALL TO CART

## RELATED GUIDES

#### Create an Internet of Things Dashboard with Adafruit IO

Visualise data measurements inside an online Adafruit IO dashboard

by M. Schwartz



In this guide you will learn how to make measurements (temperature, humidity, ambient light) with an Arduino board and send this data via WiFi to Adafruit IO. You will then be able to visualise this data in real-time, from anywhere in the world!

#### Analog Feedback Servos


# What position is your servo in? by Bill Earl



The very word "servo" implies feedback-based control. But for most RC servos, that feedback signal is not available outside the servo case. So when controlling them from a microcontroller, you never really know if the servo is doing what you tell it to do. These feedback servos have an extra wire for the feedback signal. This lets you monitor the servo motion to verify that it is working as expected. It also lets you use the servo as an input device.

# Arduino Lesson 17. Email Sending Movement Detector

novement is detected with a PIR sensor

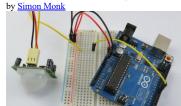

In this lesson you will learn how to use a PIR movement detector with an Arduino and to have the Arduino communicate with a Python program running on your computer to send an email whenever movement is detected by the sensor.

## 36mm LED Pixels

Big Square Glowy Dots! by Phillip Burgess





Our 36mm square pixels are our biggest and brightest! They feature four LEDs total and come in a flat metal square 'plate' that is flooded with epoxy. They require 12VDC power and can draw up to 120mA per pixel.

### OUT OF STOCK NOTIFICATION

YOUR NAME YOUR EMAIL

#### NOTIFY ME

- CONTACT
- SUPPORT
- DISTRIBUTORS
- EDUCATORS
- **JOBS**
- <u>FAO</u>
- SHIPPING & RETURNS
   TERMS OF SERVICE
   PRIVACY & LEGAL

- ABOUT US

ENGINEERED IN NYC Adafruit ®

"Flexibility is the key to stability" - John Wooden



PayPal amazon payments DISCOVER





